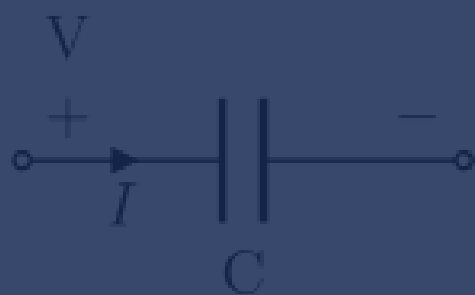



(same as normal)




Network Theory

Basic Circuit Laws, Frequency Analysis, and Network Parameters

Course Code: 3EC4-06

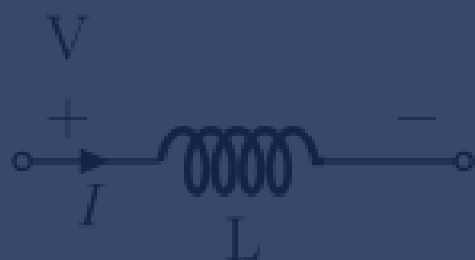

OR

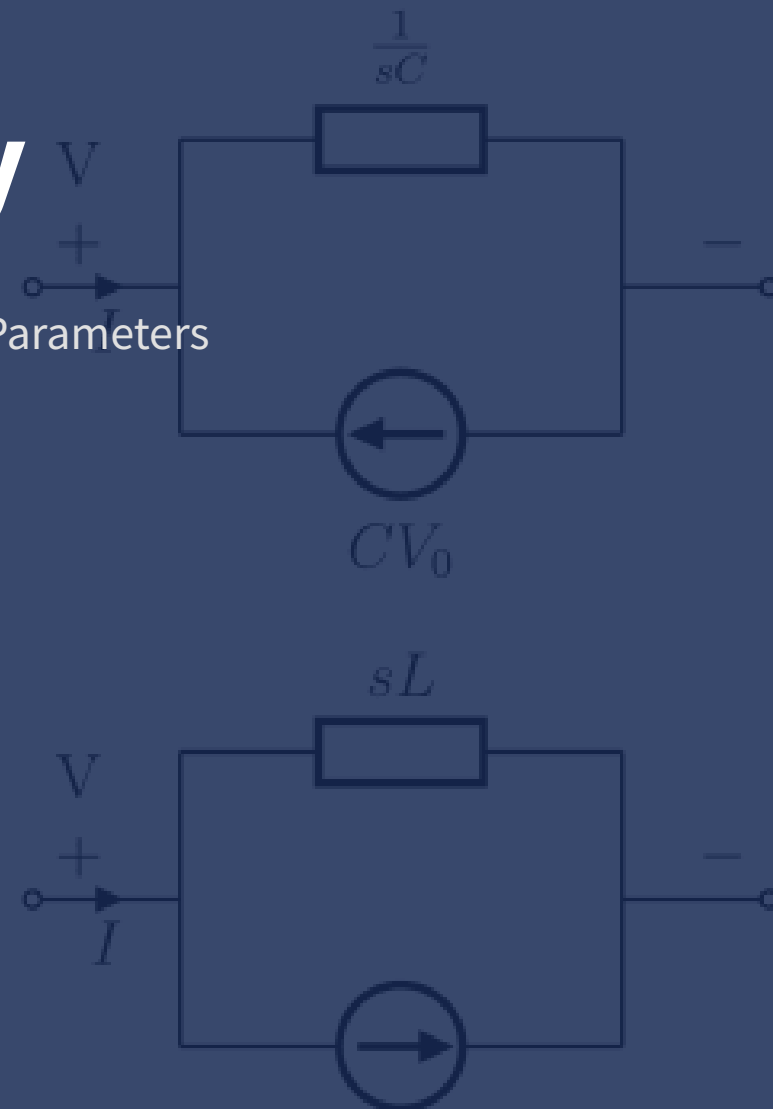

Course Overview

Network Theory (3EC4-06)

1

Network Simplification

Apply basic circuit laws and theorems for network simplification

2

Frequency-Domain Analysis

Utilize frequency-domain techniques in network analysis

3

Laplace Transforms

Perform steady-state and transient analysis using Laplace transforms

4

Two-Port Networks

Analyze transient responses and compute two-port network parameters

5

Resonance & Filters

Examine resonance conditions and design passive filters


CO-1: Basic Circuit Laws

Apply basic circuit laws and theorems for network simplification

⚡ Kirchhoff's Laws

$$\text{KCL: } \Sigma I_{\text{in}} = \Sigma I_{\text{out}}$$

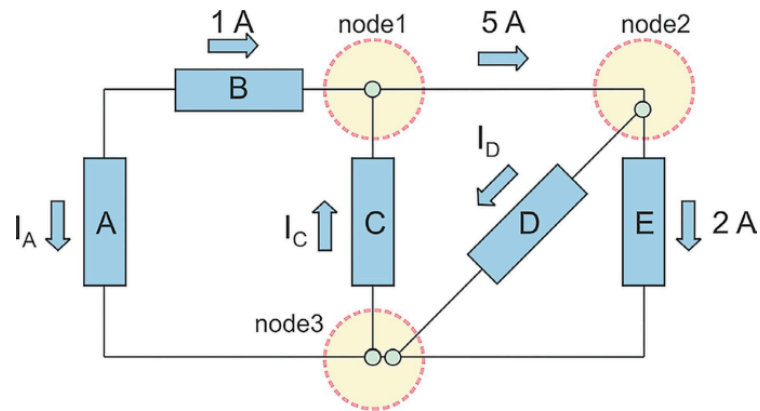Current Law: The algebraic sum of currents entering a node equals the sum of currents leaving it.




$$\text{KVL: } \Sigma V = 0 \text{ (closed loop)}$$

Voltage Law: The algebraic sum of voltages around any closed loop is zero.

🔌 Ohm's Law

$$V = I \times R$$

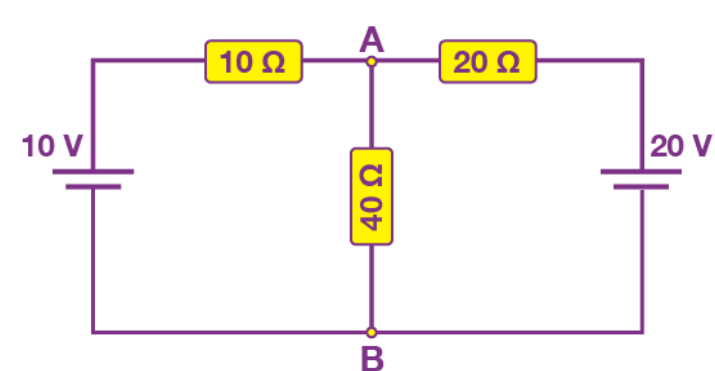The voltage across a resistor is directly proportional to the current flowing through it.



BYJU'S
The Learning App

Applications:


- Calculate voltage, current, or resistance
- Determine power dissipation: $P = V^2/R = I^2R$
- Design voltage dividers

CO-1: Network Theorems

Thevenin's and Norton's Theorems, Superposition Theorem

Thevenin's Theorem

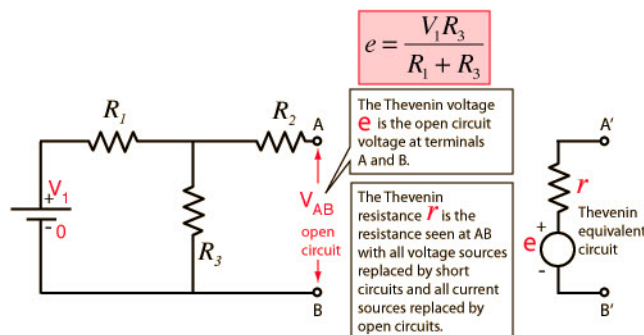
Any **linear network** can be replaced by an equivalent circuit with a single voltage source (V_{th}) in series with a resistance (R_{th}).



- 1 Remove load resistor
- 2 Calculate V_{th} (open-circuit voltage)
- 3 Calculate R_{th} (with sources replaced by their internal resistance)

Norton's Theorem

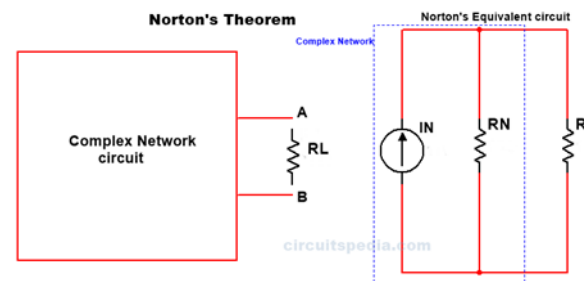
Any **linear network** can be replaced by an equivalent circuit with a current source (I_N) in parallel with a resistance (R_N).



- 1 Remove load resistor
- 2 Calculate I_N (short-circuit current)
- 3 Calculate R_N (with sources replaced by their internal resistance)

Superposition Theorem

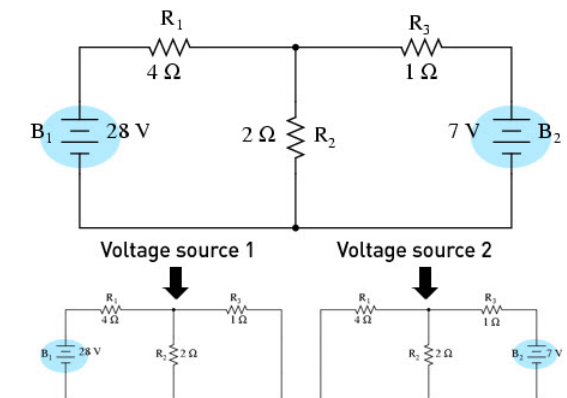In a **linear circuit** with multiple sources, the total response is the sum of individual responses from each source acting alone.



- 1 Turn off all sources except one
- 2 Calculate response (voltage/current)
- 3 Repeat for each source
- 4 Sum all individual responses


CO-1: Additional Network Theorems

Maximum Power Transfer, Millman's Theorem, and Source Transformation

⚡ Maximum Power Transfer

Maximum power is transferred from source to load when **load resistance equals source resistance**
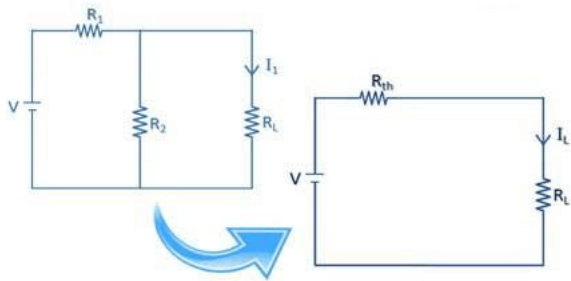
$$P_{\max} = V_{\text{th}}^2 / 4R_{\text{th}}$$




- 1 Find Thevenin equivalent circuit
- 2 Set $R_L = R_{\text{th}}$
- 3 Calculate P_{\max}

⤴ Millman's Theorem

Simplifies circuits with **multiple parallel voltage sources** into a single equivalent source
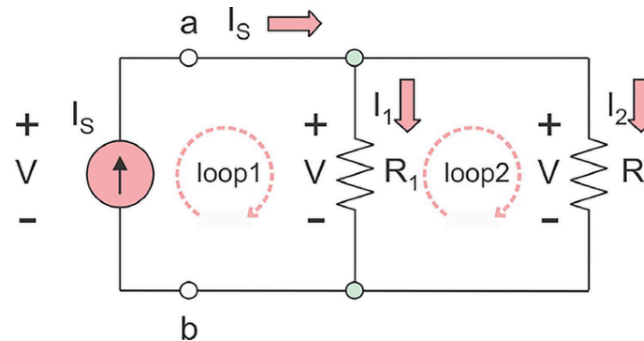
$$V_{\text{eq}} = \Sigma(V_i/R_i) / \Sigma(1/R_i)$$




- 1 Convert all sources to current sources
- 2 Sum all currents and conductances
- 3 Calculate equivalent voltage source

↔ Source Transformation

Technique to convert between **voltage and current sources** while maintaining equivalent circuit behavior

$$V_s = I_s \times R_s$$

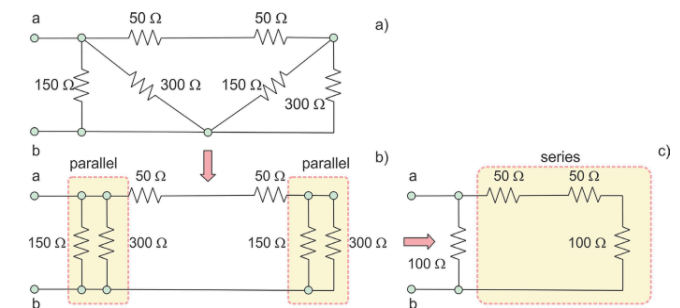

- 1 Identify source type (voltage/current)
- 2 Apply transformation formula
- 3 Simplify resulting circuit

CO-2: Frequency Domain Fundamentals

Time domain vs. frequency domain representation, phasor representation, and complex numbers in AC circuits


Time vs. Frequency Domain

Time Domain

- Signals expressed as function of time
- Direct representation of waveform
- Amplitude vs. time plot
- Transient behavior visible

Frequency Domain

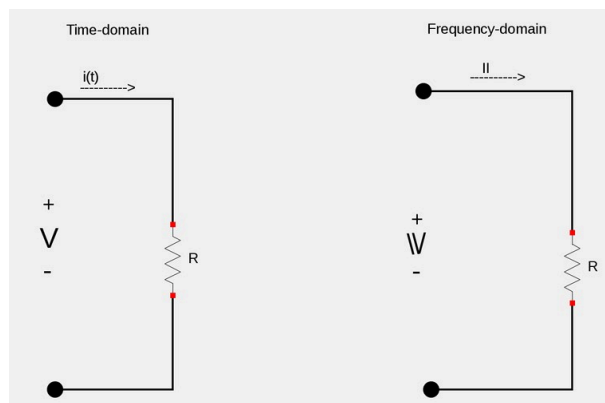
- Signals expressed as sum of sinusoids
- Amplitude and phase vs. frequency
- Simplifies AC circuit analysis
- Steady-state behavior focus



Phasor Representation

Phasor: Complex representation of sinusoidal signals in frequency domain
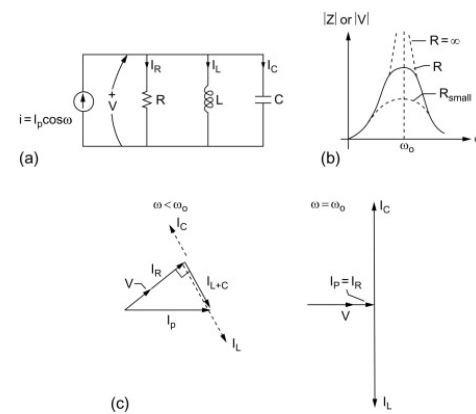
$$v(t) = V_m \cos(\omega t + \phi) \leftrightarrow \underline{V} = V_m \angle \phi$$



Key Benefits:

- Simplifies differential equations to algebraic equations
- Enables easy calculation of magnitude and phase relationships
- Reduces AC circuit analysis to DC-like methods


Complex Numbers in AC

Impedance (Z): Complex opposition to AC current

$$Z = R + jX = |Z| \angle \theta$$

Component Impedances:

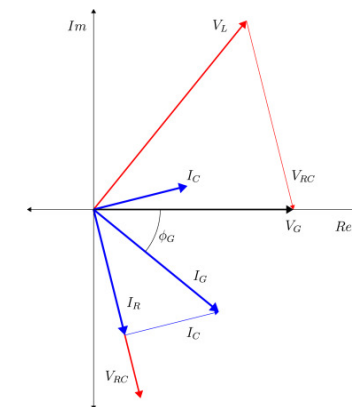- Resistor: $Z^R = R$
- Inductor: $Z^L = j\omega L$
- Capacitor: $Z^C = 1/(j\omega C)$



CO-2: Impedance and Admittance

Complex impedance, admittance in AC circuits, complex power calculations, and frequency response analysis

🔌 Complex Impedance

Impedance (Z): Total opposition to AC current flow

$$Z = R + jX = |Z| \angle \theta$$

Component Impedances:

Component	Impedance	Phase
Resistor (R)	$Z_R = R$	0°
Inductor (L)	$Z_L = j\omega L$	$+90^\circ$
Capacitor (C)	$Z_C = 1/(j\omega C)$	-90°

Key Applications:

- Simplifies AC circuit analysis
- Enables phasor-based calculations

↔ Admittance & Complex Power

Admittance (Y): Reciprocal of impedance, measures how easily current flows

$$Y = 1/Z = G + jB = |Y| \angle \phi$$

Complex Power (S):

$$S = P + jQ = V \cdot I^* = |V| |I| \angle (\theta_v - \theta_i)$$


Power Components:

- P (Real Power):** Energy consumed (W)
- Q (Reactive Power):** Energy stored/released (VAR)
- |S| (Apparent Power):** Vector sum (VA)

✓ Frequency Response

Transfer Function (H(jω)): Ratio of output to input in frequency domain

$$H(j\omega) = |H(j\omega)| \angle \phi(\omega)$$

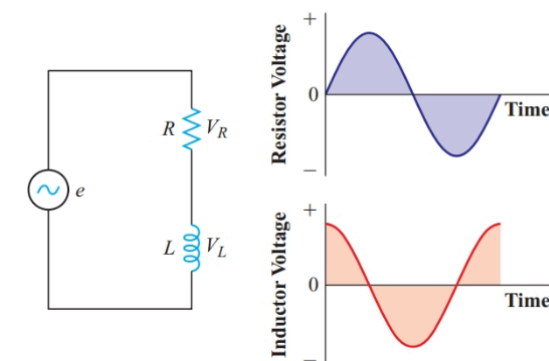

Key Metrics:

- Magnitude Response:** $|H(j\omega)|$ vs. frequency
- Phase Response:** $\phi(\omega)$ vs. frequency
- Bandwidth:** Frequency range where $\max |H(j\omega)| \geq 0.707 |H|$

CO-3: Laplace Transform Fundamentals

Definition, properties, and transformation of circuit elements to s-domain


Σ Definition & Properties

Laplace Transform: Converts time-domain functions to complex frequency domain

$$F(s) = \mathcal{L}\{f(t)\} = \int_0^{\infty} f(t)e^{-st} dt$$

Key Properties:

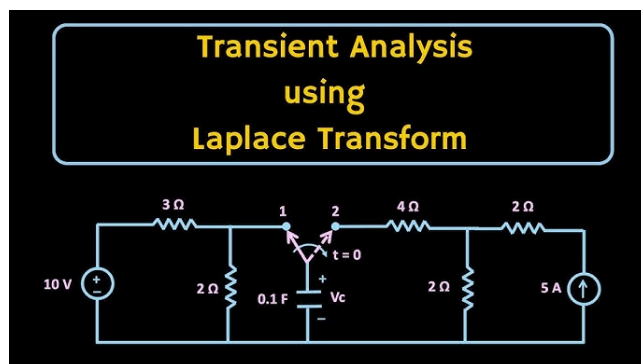
- **Linearity:** $\mathcal{L}\{af(t)+bg(t)\} = aF(s)+bG(s)$
- **Differentiation:** $\mathcal{L}\{df/dt\} = sF(s)-f(0)$
- **Integration:** $\mathcal{L}\{\int f(t)dt\} = F(s)/s$
- **Time Shift:** $\mathcal{L}\{f(t-a)u(t-a)\} = e^{-as}F(s)$



↔ Time to s-Domain

Advantages of s-Domain:

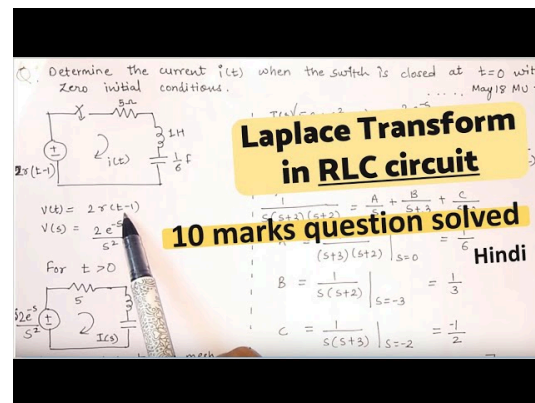- Transforms differential equations to algebraic equations
- Handles initial conditions automatically
- Enables analysis of transient and steady-state responses
- Facilitates system stability analysis




Common Transform Pairs:

- $e^{-at} \leftrightarrow 1/(s+a)$
- $\sin(\omega t) \leftrightarrow \omega/(s^2+\omega^2)$
- $\cos(\omega t) \leftrightarrow s/(s^2+\omega^2)$

⚡ Circuit Element Transformations

Transforming Circuit Elements:

Element	Time Domain	s-Domain
Resistor	$v = Ri$	$V(s) = RI(s)$
Inductor	$v = L(di/dt)$	$V(s) = sLI(s) - Li(0)$
Capacitor	$i = C(dv/dt)$	$I(s) = sCV(s) - Cv(0)$

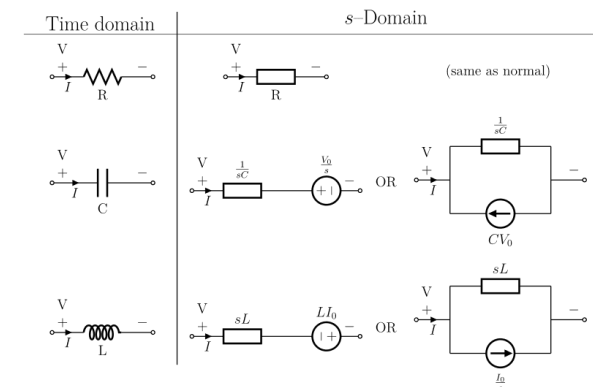

CO-3: Transient and Steady-State Analysis

Initial and final value theorems, solving differential equations using Laplace transforms, and circuit examples

Value Theorems

Initial Value Theorem: Determines $f(0+)$ from $F(s)$

$$f(0+) = \lim_{s \rightarrow \infty} sF(s)$$

Final Value Theorem: Determines $f(\infty)$ from $F(s)$

$$f(\infty) = \lim_{s \rightarrow 0} sF(s)$$

Applications:


- 1 Find initial conditions without inverse transform
- 2 Determine steady-state behavior directly
- 3 Verify circuit response at extreme conditions



Solving Differential Equations

Solution Process:

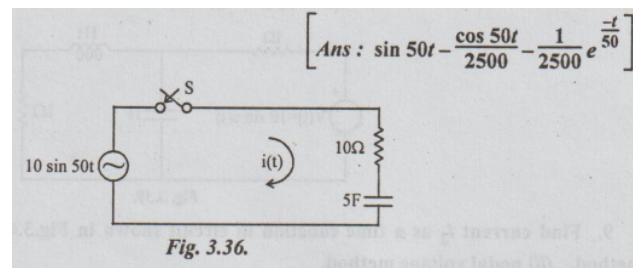- 1 Transform circuit to s-domain
- 2 Apply circuit laws in s-domain
- 3 Solve for unknown quantities
- 4 Apply inverse Laplace transform



Key Advantage: Transforms differential equations to algebraic equations

Transient & Steady-State


Response Components:

Transient Response

Temporary behavior during transition between states
Contains exponential terms with negative real parts

Steady-State Response

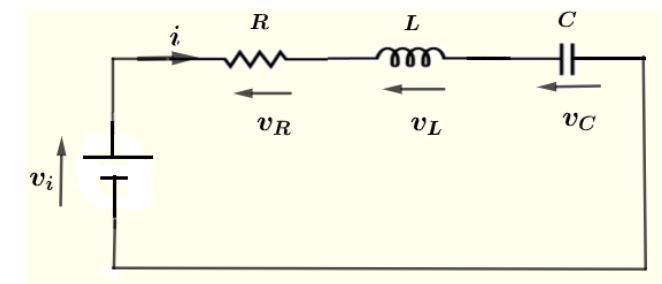Long-term behavior after transients decay
Contains sinusoidal terms at input frequency



Poles & Zeros:


- 1 Poles determine natural response and stability
- 2 Zeros affect amplitude and phase characteristics

CO-4: Two-Port Network Fundamentals

Definitions, Z-parameters (impedance parameters), and Y-parameters (admittance parameters) with circuit diagrams

Two-Port Network Basics

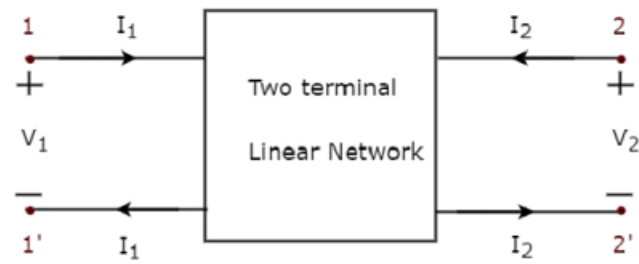Definition: Electrical network with two pairs of terminals (ports) where input is applied to one port and output is taken from the other



Key Variables:

- V_1, V_2 : Port voltages
- I_1, I_2 : Port currents
- Positive convention: Current entering the port

Applications:

- Amplifier and filter design
- Transmission line analysis
- Network interconnection

Z-Parameters

Impedance Parameters: Relate port voltages to port currents

$$\begin{aligned} V_1 &= Z_{11}I_1 + Z_{12}I_2 \\ V_2 &= Z_{21}I_1 + Z_{22}I_2 \end{aligned}$$

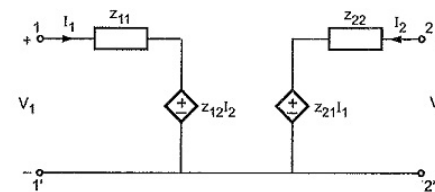


Fig. 6.3 Equivalent network of a two port network in terms of z-parameters

Parameter	Definition	Test Condition
Z_{11}	V_1/I_1	$I_2 = 0$ (open circuit)
Z_{12}	V_1/I_2	$I_1 = 0$ (open circuit)

Y-Parameters

Admittance Parameters: Relate port currents to port voltages

$$\begin{aligned} I_1 &= Y_{11}V_1 + Y_{12}V_2 \\ I_2 &= Y_{21}V_1 + Y_{22}V_2 \end{aligned}$$

	[Z]	[Y]	[T]	[T']	[h]	[g]
[Z]	$Z_{11} \quad Z_{12}$ $Z_{21} \quad Z_{22}$	$\frac{Y_{22}}{\Delta_Y} \quad \frac{Y_{12}}{\Delta_Y}$ $\frac{Y_{21}}{\Delta_Y} \quad \frac{Y_{11}}{\Delta_Y}$	$\frac{A}{C} \quad \frac{\Delta_T}{C}$ $\frac{1}{C} \quad \frac{D}{C}$	$\frac{D'}{C'} \quad \frac{1}{C'}$ $\frac{A'}{C'} \quad \frac{B'}{C'}$	$\frac{\Delta_h}{h_{22}} \quad \frac{1}{h_{22}}$ $\frac{h_{21}}{h_{22}} \quad \frac{1}{h_{22}}$	$\frac{1}{g_{22}} \quad \frac{g_{12}}{g_{22}}$ $\frac{g_{21}}{g_{22}} \quad \frac{1}{g_{22}}$
[Y]	$\frac{Z_{22}}{\Delta_Z} \quad \frac{-Z_{12}}{\Delta_Z}$ $\frac{-Z_{21}}{\Delta_Z} \quad \frac{Z_{11}}{\Delta_Z}$	$Y_{11} \quad Y_{12}$ $Y_{21} \quad Y_{22}$	$\frac{D}{B} \quad \frac{\Delta_T}{B}$ $\frac{1}{B} \quad \frac{A}{B}$	$\frac{A'}{B'} \quad \frac{1}{B'}$ $\frac{D'}{B'} \quad \frac{C'}{B'}$	$\frac{1}{h_{11}} \quad \frac{h_{12}}{h_{11}}$ $\frac{h_{21}}{h_{11}} \quad \frac{\Delta_h}{h_{11}}$	$\frac{\Delta_g}{g_{22}} \quad \frac{g_{12}}{g_{22}}$ $\frac{g_{21}}{g_{22}} \quad \frac{1}{g_{22}}$
[T]	$\frac{Z_{11}}{\Delta_Z} \quad \frac{\Delta_Z}{\Delta_Z}$ $\frac{Z_{21}}{\Delta_Z} \quad \frac{1}{\Delta_Z}$	$\frac{Y_{22}}{\Delta_Y} \quad \frac{1}{\Delta_Y}$ $\frac{Y_{21}}{\Delta_Y} \quad \frac{Y_{11}}{\Delta_Y}$	$A \quad B$ $C \quad D$	$\frac{D'}{C'} \quad \frac{B'}{C'}$ $\frac{A'}{C'} \quad \frac{1}{C'}$	$\frac{\Delta_h}{h_{22}} \quad \frac{h_{11}}{h_{22}}$ $\frac{h_{21}}{h_{22}} \quad \frac{1}{h_{22}}$	$\frac{1}{g_{22}} \quad \frac{g_{12}}{g_{22}}$ $\frac{g_{21}}{g_{22}} \quad \frac{1}{g_{22}}$
[T']	$\frac{Z_{22}}{\Delta_Z} \quad \frac{\Delta_Z}{\Delta_Z}$ $\frac{1}{\Delta_Z} \quad \frac{Z_{11}}{\Delta_Z}$	$\frac{Y_{11}}{\Delta_Y} \quad \frac{1}{\Delta_Y}$ $\frac{Y_{12}}{\Delta_Y} \quad \frac{Y_{21}}{\Delta_Y}$	$\frac{D}{\Delta_T} \quad \frac{B}{\Delta_T}$ $\frac{C}{\Delta_T} \quad \frac{A}{\Delta_T}$	$\frac{A'}{C'} \quad \frac{B'}{C'}$ $\frac{D'}{C'} \quad \frac{1}{C'}$	$\frac{1}{h_{11}} \quad \frac{\Delta_h}{h_{11}}$ $\frac{h_{21}}{h_{11}} \quad \frac{g_{12}}{h_{11}}$	$\frac{g_{22}}{g_{11}} \quad \frac{g_{12}}{g_{11}}$ $\frac{1}{g_{11}} \quad \frac{1}{g_{11}}$
[h]	$\frac{\Delta_Z}{Z_{11}} \quad \frac{Z_{12}}{Z_{11}}$ $\frac{Z_{21}}{Z_{11}} \quad \frac{1}{Z_{11}}$	$\frac{Y_{22}}{\Delta_Y} \quad \frac{1}{\Delta_Y}$ $\frac{Y_{21}}{\Delta_Y} \quad \frac{Y_{11}}{\Delta_Y}$	$\frac{B}{D} \quad \frac{\Delta_T}{D}$ $\frac{1}{D} \quad \frac{C}{D}$	$\frac{B'}{A'} \quad \frac{1}{A'}$ $\frac{D'}{A'} \quad \frac{C'}{A'}$	$\frac{h_{12}}{h_{22}} \quad \frac{h_{11}}{h_{22}}$ $\frac{h_{21}}{h_{22}} \quad \frac{1}{h_{22}}$	$\frac{g_{22}}{g_{11}} \quad \frac{g_{12}}{g_{11}}$ $\frac{g_{21}}{g_{11}} \quad \frac{1}{g_{11}}$
[g]	$\frac{1}{Z_{11}} \quad \frac{Z_{12}}{Z_{11}}$ $\frac{Z_{21}}{Z_{11}} \quad \frac{1}{Z_{11}}$	$\frac{Y_{22}}{\Delta_Y} \quad \frac{1}{\Delta_Y}$ $\frac{Y_{21}}{\Delta_Y} \quad \frac{Y_{11}}{\Delta_Y}$	$\frac{C}{A} \quad \frac{\Delta_T}{A}$ $\frac{1}{A} \quad \frac{B}{A}$	$\frac{C'}{A'} \quad \frac{\Delta_T}{A'}$ $\frac{1}{A'} \quad \frac{B'}{A'}$	$\frac{h_{22}}{\Delta_h} \quad \frac{h_{12}}{\Delta_h}$ $\frac{h_{21}}{\Delta_h} \quad \frac{1}{\Delta_h}$	$\frac{g_{11}}{g_{22}} \quad \frac{g_{12}}{g_{22}}$ $\frac{g_{21}}{g_{22}} \quad \frac{1}{g_{22}}$

Parameter	Definition	Test Condition
Y_{11}	I_1/V_1	$V_2 = 0$ (short circuit)
Y_{12}	I_1/V_2	$V_1 = 0$ (short circuit)

CO-4: Additional Two-Port Parameters

H-parameters (hybrid parameters), Transmission parameters (ABCD parameters), and interconnection of two-port networks

↔ H-Parameters

Hybrid Parameters: Mix of impedance and admittance parameters

$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

NAME	EXPRESS	IN TERMS OF	DEFINING EQUATIONS
Impedance	V_1, V_2	I_1, I_2	$V_1 = z_{11}I_1 + z_{12}I_2$ and $V_2 = z_{21}I_1 + z_{22}I_2$
Admittance	I_1, I_2	V_1, V_2	$I_1 = y_{11}V_1 + y_{12}V_2$ and $I_2 = y_{21}V_1 + y_{22}V_2$
Hybrid	V_1, I_2	I_1, V_2	$V_1 = h_{11}I_1 + h_{12}V_2$ and $I_2 = h_{21}I_1 + h_{22}V_2$
Transmission	V_1, I_1	$V_2, -I_2$	$V_1 = A V_2 - B I_2$ and $I_1 = C V_2 - D I_2$

Parameter	Definition	Test Condition
h_{11}	V_1/I_1	$V_2 = 0$ (short circuit)
h_{21}	I_2/I_1	$V_2 = 0$ (short circuit)

Applications: Transistor modeling


⇒ Transmission Parameters

ABCD Parameters: Relate input voltage/current to output voltage/current

$$V_1 = AV_2 + BI_2$$

$$I_1 = CV_2 + DI_2$$

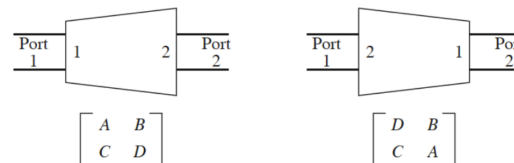ABCD matrix representation is $\begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_1 \\ I_1 \end{bmatrix}$
a. For the ABCD network shown below prove that reversing the network causes the ABCD parameters to change as indicated.



Parameter	Definition	Test Condition
A	V_1/V_2	$I_2 = 0$ (open circuit)
D	I_1/I_2	$V_2 = 0$ (short circuit)

Applications: Transmission lines, cascaded networks

👤 Network Interconnection

Series Connection: Port 2 of first network connects to port 1 of second network

- Z-parameters: $Z = Z^A + Z^B$
- Used for cascaded amplifiers

Parallel Connection: Both ports of networks connected in parallel

- Y-parameters: $Y = Y^A + Y^B$
- Used for parallel filters

Cascade Connection:

- ABCD-parameters: $T = T^A \times T^B$
- Used for transmission lines


CO-5: Resonance in RLC Circuits

Series and parallel resonance, resonant frequency, quality factor, and frequency response curves

Series Resonance

Condition: $X_L = X_C$

$$\omega_0 = 1/\sqrt{LC}$$

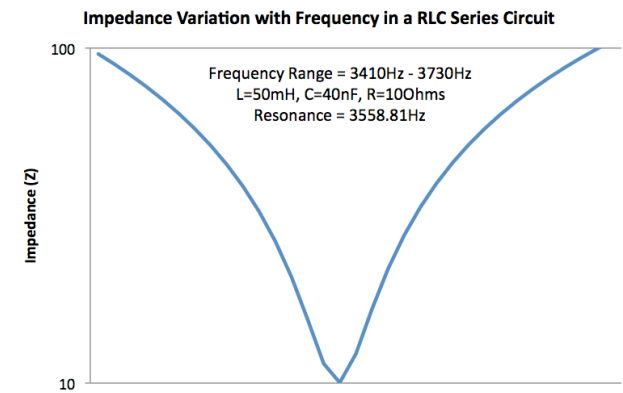


Parameter	Value at Resonance
Impedance (Z)	Minimum = R
Current (I)	Maximum = V/R
Power Factor	Unity (1)

Parallel Resonance

Condition: $B_L = B_C$

$$\omega_0 = 1/\sqrt{LC}$$

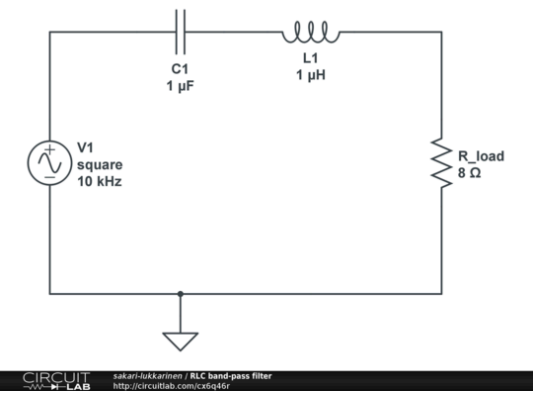

Parameter	Value at Resonance
Impedance (Z)	Maximum
Current (I)	Minimum
Power Factor	Unity (1)

Quality Factor & Bandwidth

Quality Factor (Q): Measure of selectivity

$$Q = \omega_0 L / R = 1 / (\omega_0 RC)$$

Bandwidth (BW): Frequency range where response ≥ 0.707 of maximum

$$BW = \omega_0 / Q$$


Applications:

- Radio tuning circuits
- Signal filtering
- Oscillator design
- Power factor correction


CO-5: Passive Filter Design

Low-pass, high-pass, band-pass, and band-stop filters with circuit diagrams and frequency response characteristics

↓ Low-Pass Filter

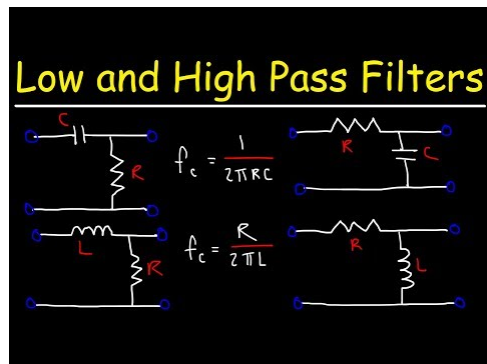


$$f_c = 1/(2\pi RC)$$

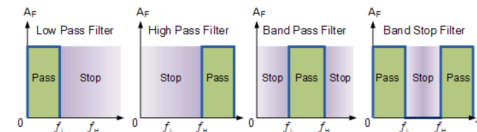


- **Function:** Passes low frequencies, attenuates high frequencies
- **Applications:** Audio systems, anti-aliasing, power supplies

↑ High-Pass Filter

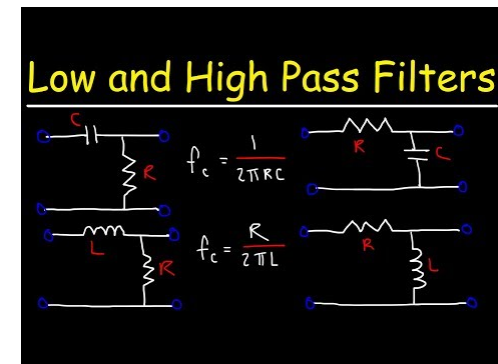


$$f_c = 1/(2\pi RC)$$

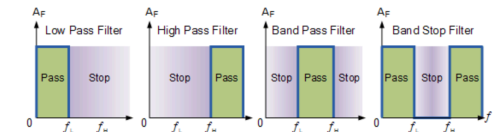


- **Function:** Passes high frequencies, attenuates low frequencies
- **Applications:** Audio crossovers, AC coupling, DC blocking

→ Band-Pass Filter

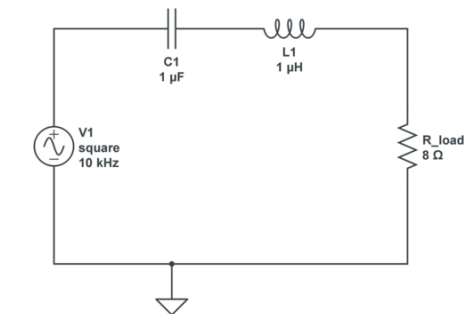


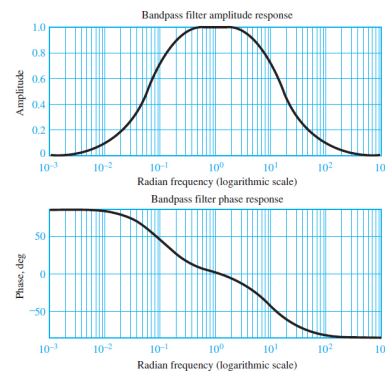
CIRCUIT LAB
safari-lukkarinen / RLC band-pass filter
http://circuitlab.com/cx/dg46r



- **Function:** Passes frequencies within a specific band
- **Applications:** Radio tuning, audio equalizers, communication systems

$$f_0 = 1/(2\pi\sqrt{LC})$$

⊘ Band-Stop (Notch) Filter

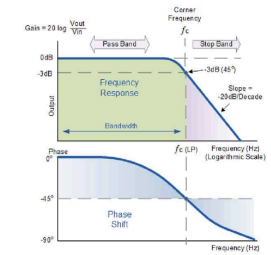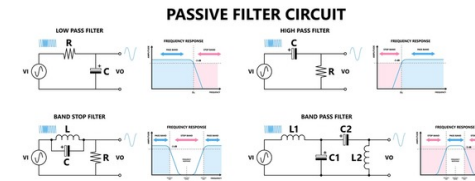

- **Function:** Rejects frequencies within a specific band
- **Applications:** Noise cancellation, harmonic filtering, audio systems

$$f_0 = 1/(2\pi\sqrt{LC})$$

Summary

Key concepts and interconnections in Network Theory

⚡ Network Simplification

- **Kirchhoff's Laws:** Current and voltage conservation
- **Thevenin/Norton:** Equivalent circuit representations
- **Superposition:** Linear response to multiple sources
- **Maximum Power Transfer:** $R_L = R_{th}$

🌊 Frequency Domain Analysis

- **Phasors:** Complex representation of sinusoids
- **Impedance/Admittance:** $Z = R + jX$, $Y = G + jB$
- **Complex Power:** $S = P + jQ = V \cdot I^*$
- **Frequency Response:** $H(j\omega) = |H(j\omega)| \angle \phi(\omega)$

Σ Laplace Transform Analysis

- **Transform:** $F(s) = \int f(t)e^{-st}dt$
- **Circuit Elements:** $R \rightarrow R$, $L \rightarrow sL$, $C \rightarrow 1/sC$
- **Value Theorems:** Initial/final values from $F(s)$
- **Transient/Steady State:** Natural and forced responses

🔗 Two-Port Networks

- **Z-Parameters:** $V = Z \cdot I$ (impedance)
- **Y-Parameters:** $I = Y \cdot V$ (admittance)
- **H-Parameters:** Mixed impedance/admittance
- **ABCD-Parameters:** Transmission parameters

⚡ Resonance & Filters

- **Resonance:** $\omega^0 = 1/\sqrt{LC}$
- **Quality Factor:** $Q = \omega^0 L/R$
- **Filter Types:** LP, HP, BP, BS
- **Frequency Response:** Passband/stopband characteristics

🔗 Key Interconnections

Simplification → Analysis

Network theorems enable complex circuit simplification before applying frequency or Laplace domain analysis

Frequency → Laplace

Laplace transforms extend frequency domain analysis to include transient responses and initial conditions

Two-Port → Filters

Two-port network parameters provide systematic methods for filter design and cascade connection

Thank You

For your attention to this Network Theory presentation

Contact Information

 instructor@university.edu

 +1 (123) 456-7890

 Office Hours: Mon/Wed 2-4 PM

 Engineering Building, Room 312

Further Study

- Network Analysis - M.E. Van Valkenburg
- Engineering Circuit Analysis - Hayt, Kemmerly, Durbin
- Network Theory - N. C. Jagan & C. Lakshmi
- Network Theory - A. Sudhakar & Shyammohan S. Palli
- IEEE Transactions on Circuits and Systems